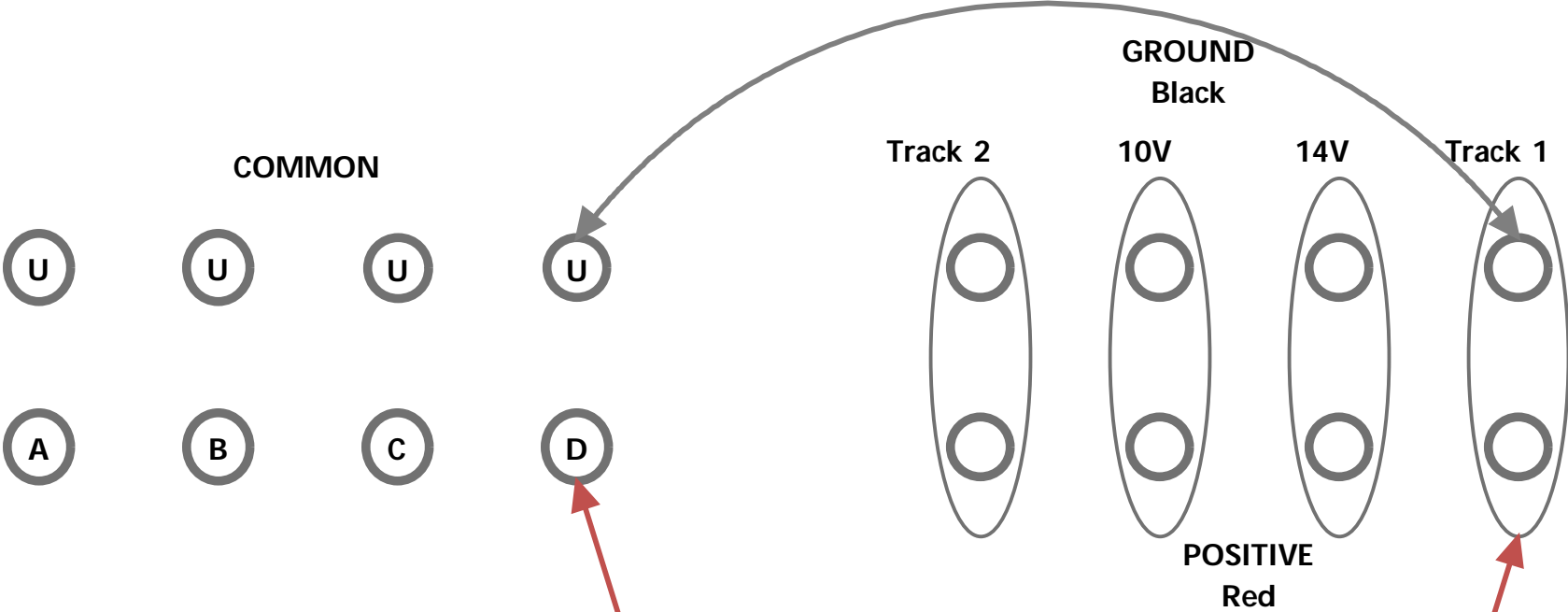


# Phase Lionel Postwar ZW with MTH Z4000

Postwar ZW Low Voltage Terminals

MTH Z4000 Low Voltage Terminals



Set ZW D handle at 14V.  
Set Z400 Track 1 handle at 14V  
Measure Voltage between the ZW D voltage post and Track 2 voltage post on Z4000. Or place a 14V lamp between the two posts. There should be no more that one or two volts showing on the voltmeter. OR, the lamp doesn't light.